

TUTORIAL 1

(B.Tech, IInd Sem, Electronics Engg.)


1. If the base current in transistor is $30 \mu\text{A}$ when the emitter current is 7.2 mA . What are the values of α and β ($\beta=239, \alpha=0.9958$)
2. In a CE transistor amplifier circuit V_{CE} is increased from 2 to 12 V , the collector current changes from 3 mA to 4 mA , determine the output resistance. ($10 \text{ K}\Omega$)
3. In an npn transistor $\alpha=0.98$, $I_E=10 \text{ mA}$ and leakage current $I_{CBO}=1 \mu\text{A}$. Determine I_C , I_B and I_{CE0} (9.801 mA , 0.199 mA , $50 \mu\text{A}$)
4. Find the value of base current if the common-base d.c. current gain of a transistor is 0.987 and emitter current is 10 mA . (0.13 mA)
5. The collector and base current of npn transistor are measured as $I_C=5 \text{ mA}$, $I_B=50 \mu\text{A}$ and $I_{CBO}=1 \mu\text{A}$.
 (i) Determine α , β and I_E (i) $\alpha=0.99, \beta=100$ and $I_E=10.1 \text{ mA}$ (ii)
 (ii) Determine the new level of I_B required to produce $I_C=10 \text{ mA}$.
6. The value of β for a transistor is 100 . If the value of emitter current is 10 mA , then determine the value of collector and base currents. ($I_B=0.099 \text{ mA}$, $I_C=9.9 \text{ mA}$)
7. The value of α for a transistor is 0.95 . Find value of β . Also find the value of α if β changes to 100 . ($\beta=19, \alpha=0.99$)
8. Given that $\alpha_{dc}=0.987$ determine the corresponding value of β_{dc} . (75.92)
9. Given $\beta_{dc}=120$, determine the corresponding value of α . (0.9917)
10. An npn transistor connected in CE configuration has $\beta=100$ and base to collector leakage current $I_{CBO}=4 \mu\text{A}$. Calculate I_C if $I_B=40 \mu\text{A}$. (4.404 mA)
11. A transistor has $\Delta I_C=1.8 \text{ mA}$ for $\Delta I_E=1.89 \text{ mA}$, what change in I_B will produce an equivalent change in I_B . ($90 \mu\text{A}$)
12. A transistor is connected in CB configuration, when the emitter voltage is changed by 200 mV , the emitter current changes by 5 mA . During this variation, the collector to base voltage is kept fixed. Calculate the dynamic input resistance of transistor. (40Ω)
13. If the emitter current of a transistor is 8 mA and I_B is $1/100$ of I_C , determine I_C and I_B . ($I_C=7.92 \text{ mA}$, $I_B=0.08 \text{ mA}$)
14. Find I_E if $I_B=40 \mu\text{A}$ and α_{dc} is 0.98 . (2 mA)
15. In CB configuration, collector current is 0.96 mA and base current is $40 \mu\text{A}$. Determine α and I_E . ($\alpha=0.96, I_E=1 \text{ mA}$)

$$I_C = (1 + \beta) I_B$$

$$I_C = \beta I_B$$

TUTORIAL NO. 2

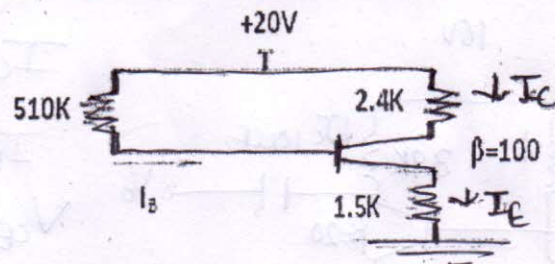Q1. Determine I_B , I_C , V_E , V_C , V_B and V_{CE} for the following circuit.



$$I_B = 29.176 \mu A$$

$$I_C = 2.9176 \text{ mA}$$


$$I_E = 2.9467 \text{ mA}$$

$$V_E = 4.42 \text{ V}$$

$$V_{CE} = 8.577 \text{ V}$$

$$V_B = 5.12 \text{ V}, V_C = 12.997 \text{ V}, V_{BC} = -7.877 \text{ V}$$

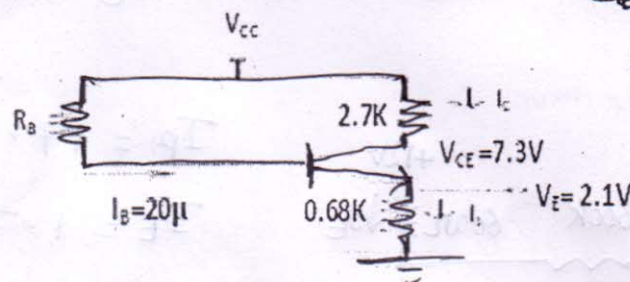Q2. Find the value of β , V_{CC} and R_B for the following circuit.



$$I_E = 3.088 \text{ mA}$$


$$\beta = 153.4$$

$$I_C = 3.068 \text{ mA}$$

$$V_{CC} = 17.68 \text{ V}$$

$$R_B = 744 \text{ K}\Omega$$

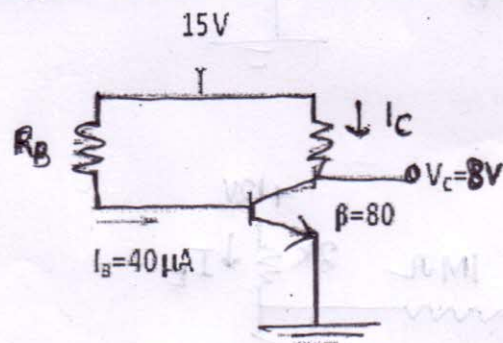Q3. Determine following for the given circuit. Assume it silicon transistor: (i) I_C (ii) V_{CE} (iii) R_C (iv) R_B



$$I_C = 3.2 \text{ mA}$$

$$R_C = 2.187 \text{ K}\Omega$$

$$R_B = 357.5 \text{ K}\Omega$$

$$V_{CE} = 8 \text{ V}$$



Q4. Draw the dc load line and locate the operating point for the circuit shown in fig. What will be its stability factor? $V_{BE} = 0.7 \text{ V}$

$$I_B = 17.439 \mu A$$


$$I_C = 2.0868 \text{ mA}$$

$$V_{CE} = 5.192 \text{ V}$$

$$S = 121$$

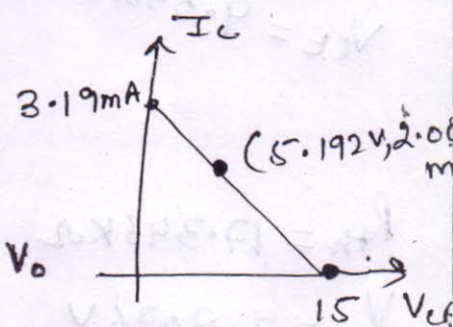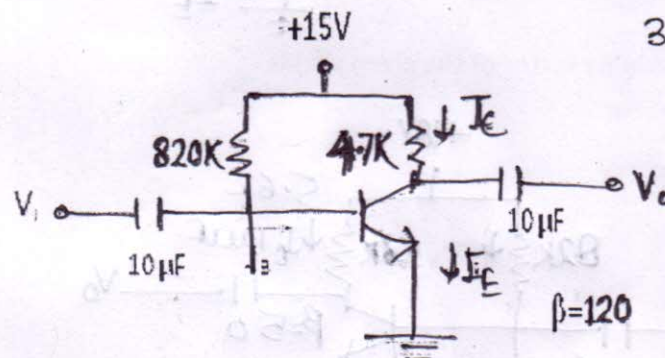

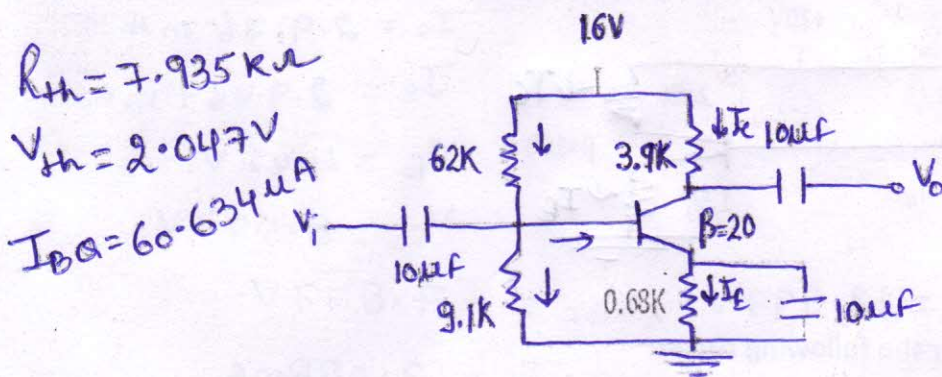Q5. Determine following for the given circuit. Assume it silicon transistor: (i) I_{BQ} and I_{CQ} (ii) V_{CEQ} (iii) V_E & V_C



$$R_{th} = 7.935 K\Omega$$

$$V_{th} = 2.047 V$$

$$I_{BQ} = 60.634 \mu A$$

$$I_{CQ} = 1.212 mA$$


$$I_E = 1.273 mA$$

$$V_{CE} = 10.407 V$$

$$V_E = 0.865 V$$

$$V_C = 11.272 V$$

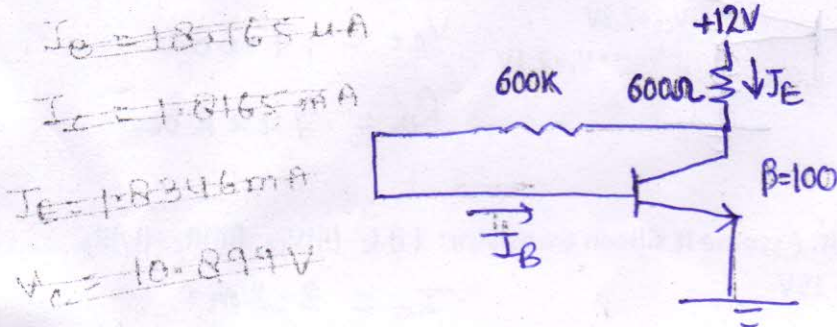Q6. Determine I_E and V_C for the given circuit.



$$I_B = 18.165 \mu A$$

$$I_C = 1.8165 mA$$

$$I_E = 1.8346 mA$$


$$V_{CE} = 10.899 V$$

$$I_B = 17.105 \mu A$$

$$I_E = 1.7276 mA$$

$$V_{CE} = 10.96 V$$

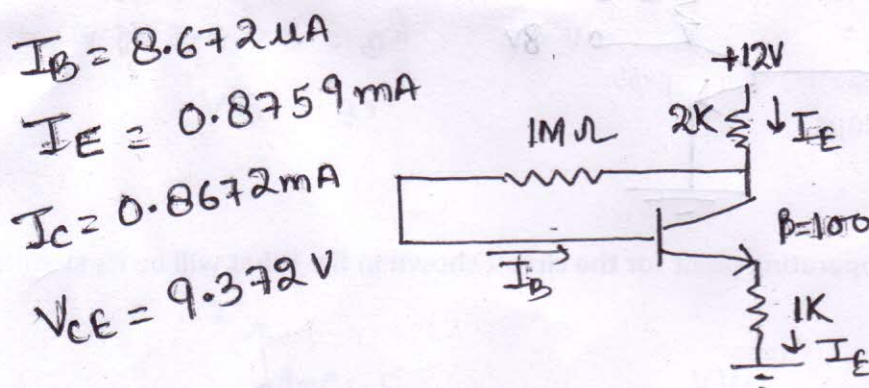Q7. Determine I_E , I_B , I_C and V_{CE} for the given circuit.




$$I_B = 8.672 \mu A$$

$$I_E = 0.8759 mA$$

$$I_C = 0.8672 mA$$

$$V_{CE} = 9.372 V$$

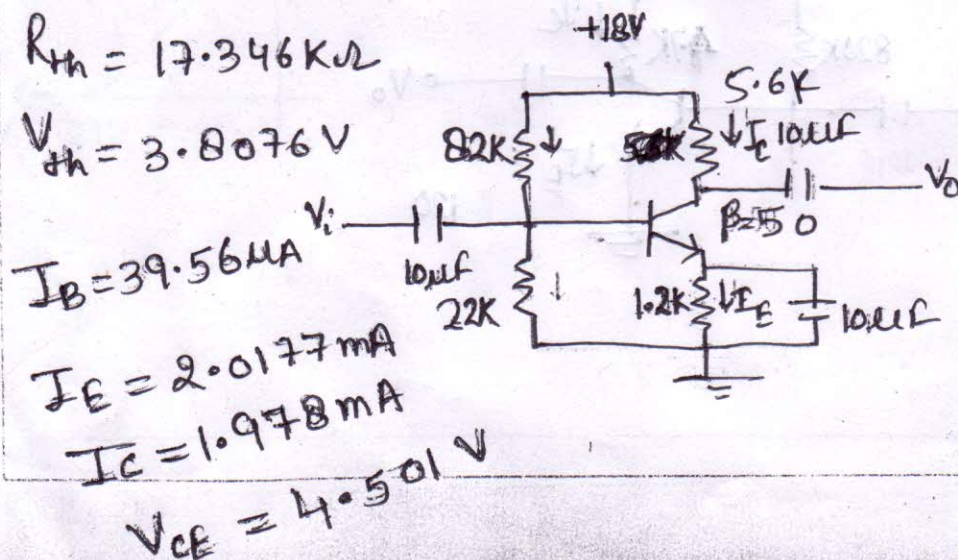Q8. Determine Q-point and stability factor of the given circuit.



$$R_{th} = 17.346 K\Omega$$

$$V_{th} = 3.8076 V$$

$$I_B = 39.56 \mu A$$

$$I_E = 2.0177 mA$$

$$I_C = 1.978 mA$$

$$V_{CE} = 4.501 V$$

1. Determine the following for the fixed-bias configuration.

a. I_{BQ} and I_{CQ}

b. V_{CEQ}

c. V_B and V_C

d. V_{BC} ($47.08 \mu A, 2.35 mA, 6.82 V, 0.7 V, 6.82 V$)

2. For the network determine

a. $V_{CE} = 11.213 V$

$I_B = 0.01545 mA$
 $= 15.45 \mu A$ or

b. $V_{CE} = 11.213 V$

c. $V_B = 0.7 V$

$I_C = 1.8547 mA$

d. $V_{BC} = -10.513 V$

$I_E = 1.8694 mA$

e. $V_E = 0 V$

f. V_{BC} ($0.725 V, 0.725 V, 0.7 V, 0.725 V, 0 V, -0.025 V$)

3. For the emitter bias network determine:

a. $I_B = 0.04012 mA = 40.12 \mu A$

b. $I_C = 2.006 mA, I_E = 2.046 mA$

c. $V_{CE} = 13.94 V$

d. $V_C = 15.98 V$



e. $V_E = 2.046 V$

$V_{BC} = -13.23 V$

f. $V_B = 2.746 V$

g. V_{BC} ($36.27 \mu A, 1.81 mA, 14.53 V, 16.38 V, 1.85 V, 2.55 V, -13.83 V$)

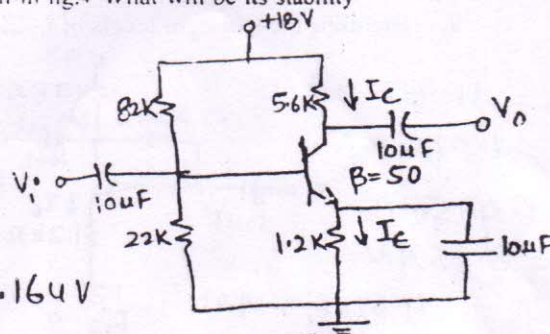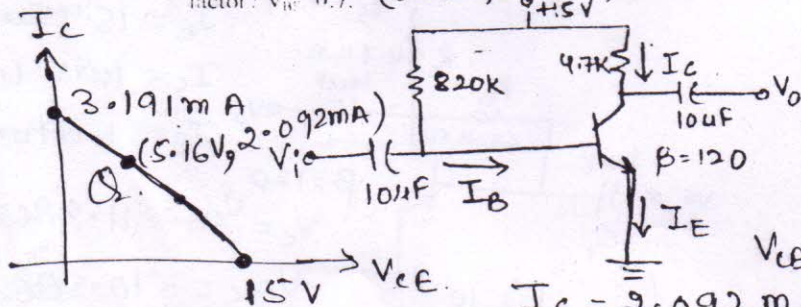4. Draw the dc load line and locate the operating for the circuit shown in fig.4 What will be its stability factor? $V_{BE} = 0.7$. ($5.082 V, 2.11 mA$)



5. Determine the levels of I_{CQ} and V_{CEQ} for the voltage-divider configuration.

($1.98 mA, 4.5 V$)

6. The load line is given in the fig.6 and the Q point is defined.

Q5 (Ans)

$$R_{th} = 17.346 K \Omega$$

$$V_{th} = 3.807 V$$

$$I_{BQ} = 0.03955 mA$$

$$= 39.55 \mu A$$

$$I_{CQ} = 1.977 mA$$

$$I_{EQ} = 2.017 mA$$

$$V_{CEQ} = 4.508 V$$

Determine the required values of V_{CC} , R_C and R_B for a fixed bias configuration.

$$(20V, 2k\Omega, 772k\Omega)$$

7. Determine the dc level of I_B and V_C for the network.

$$I_C = 2.645mA, I_E = 2.680mA$$

$$V_C = 9.156V$$

$$I_B = 35.26\mu A, V_{CE} = 7.78V$$

8. Determine the dc bias voltage V_{CE} and the current I_C for the voltage-divider configuration of fig.8.

$$I_B = 6.045\mu A$$

$$I_E = 0.852mA$$

$$I_C = 0.846mA$$

$$V_{CE} = 12.22V, 0.85mA$$

9. Determine the Quiescent levels of I_{CQ} and V_{CEQ} for the network of fig.9.

$$I_B = 11.82\mu A$$

$$I_C = 1.064mA$$

$$I_E = 1.075mA$$

$$V_{CE} = 3.657V$$

$$(1.07mA, 3.69V)$$

Fig 9

10. For the network of fig.10 determine:

(a) I_{CQ} and V_{CEQ}

(b) V_B, V_C, V_E and V_{BC}

11. Determine V_C and V_B for the network of fig.11.

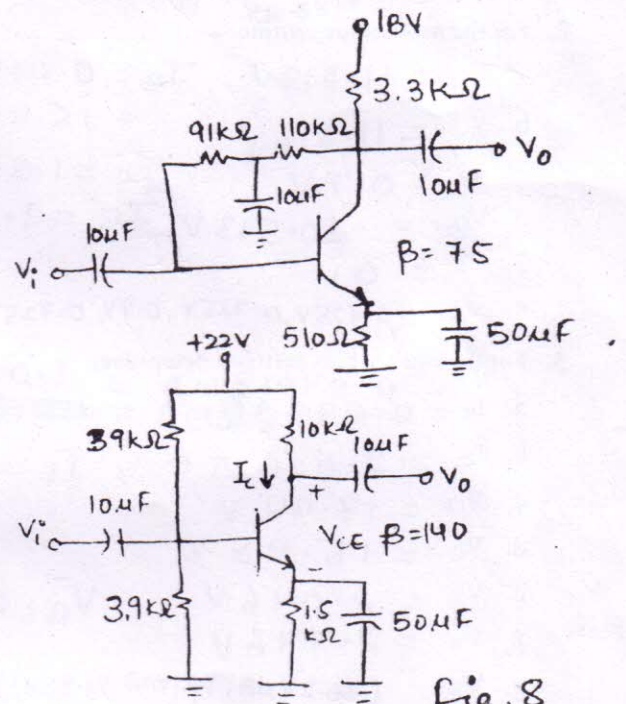
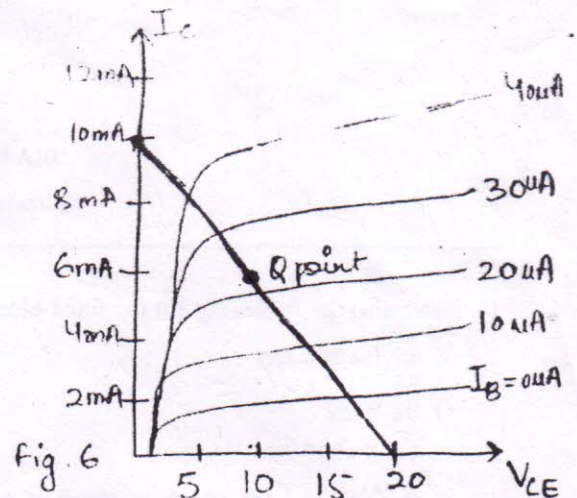


Fig. 8


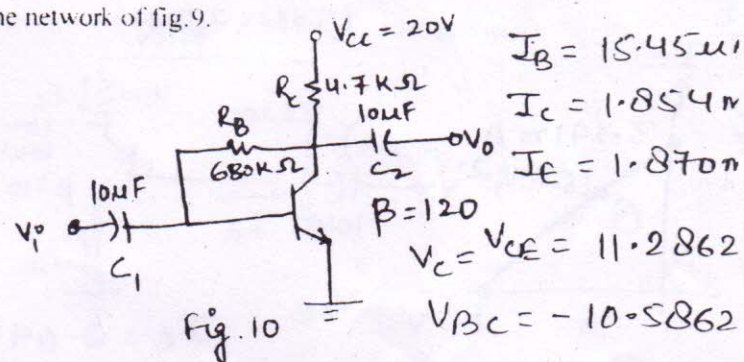


Fig. 10

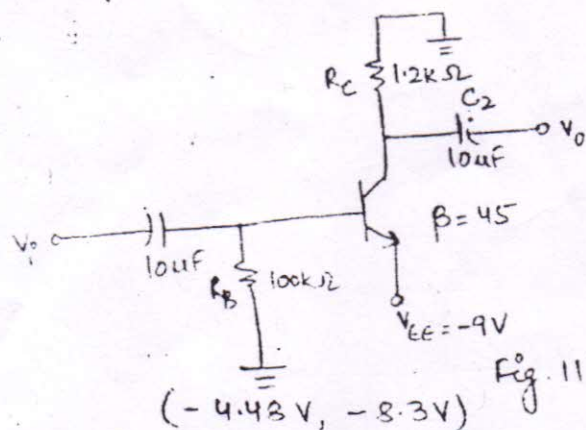



$$\begin{aligned}
 I_B &= 83 \mu A \\
 I_C &= 3.735 \text{ mA} \\
 I_E &= 3.818 \text{ mA} \\
 V_E &= -9 \text{ V} \\
 V_C &= -4.482 \text{ V} \\
 V_B &= -8.3 \text{ V}
 \end{aligned}$$

12. Determine V_{CEQ} and I_E for the network of fig. 12.

$$\begin{aligned}
 I_B &= 45.73 \mu A \\
 I_C &= 4.116 \text{ mA} \\
 I_E &= 4.161 \text{ mA} \\
 V_{CE} &= 11.678 \text{ V} \\
 & (11.68 \text{ V}, 4.16 \text{ mA})
 \end{aligned}$$

13. Determine V_E and V_B for the network of fig. 13.

Solve Question of Boylestad.

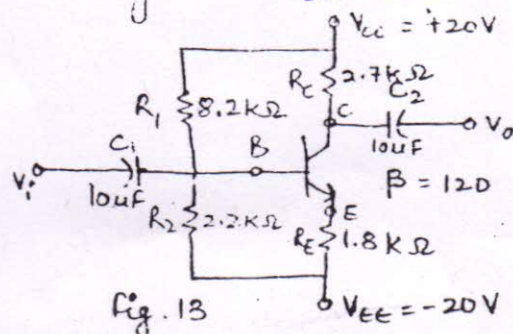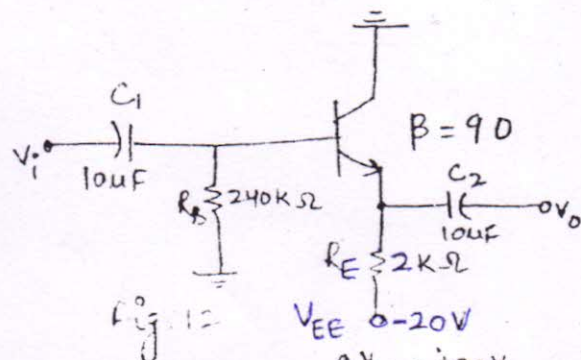



Q14 $(8.53 \text{ V}, -11.59 \text{ V})$

14. In a CE germanium transistor amplifier, voltage divider is used. Determine the following:

- The operating point
- The stability factor, S .

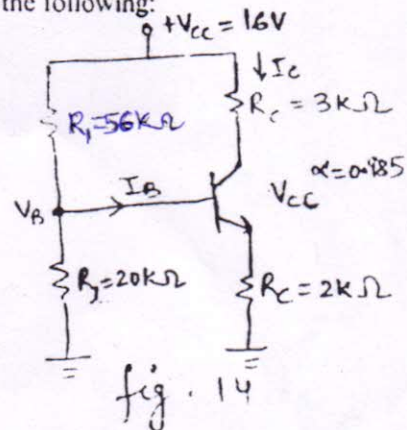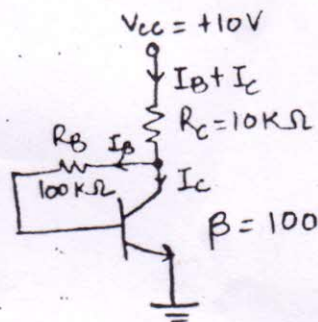15. Fig. 15 shows the collector-to-base bias circuit with $\beta = 100$. Assuming $V_{BE} = 0$, determine the following:

- The value of I_B
- The value of I_C
- The value of V_{CE}
- The stability factor



$$(9 \mu A, 0.9 \text{ mA}, 1 \text{ V}, 92.5)$$

$$\begin{aligned}
 I_B &= 9.01 \mu A \approx 9 \mu A \\
 I_C &= 0.9 \text{ mA} \\
 I_E &= 0.909 \text{ mA} \\
 V_{CE} &= 0.91 \text{ V} \\
 S &= 10.009
 \end{aligned}$$